


# S-EEG Sensor

The dsign of eeg circuit in  
multism +breadboard +PCB


# EEG Sensor

(electroencephalography)

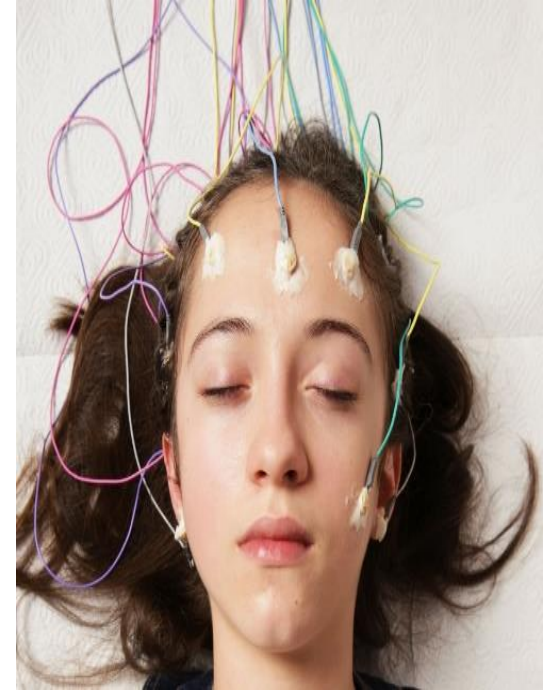
1. It is a test used to evaluate the electrical activity in the brain.
2. Brain cells communicate with each other through electrical impulses.
3. Scalp EEG recording displays the difference in electrical potentials between two different sites on the head


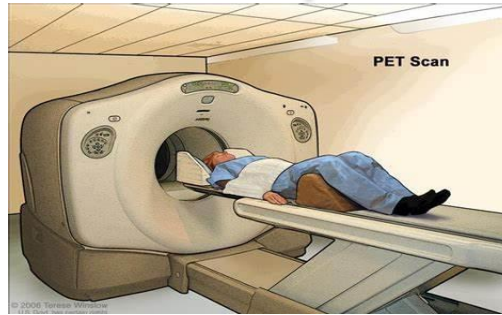
# EEG compared to other brain imaging techniques



# EEG Advantages

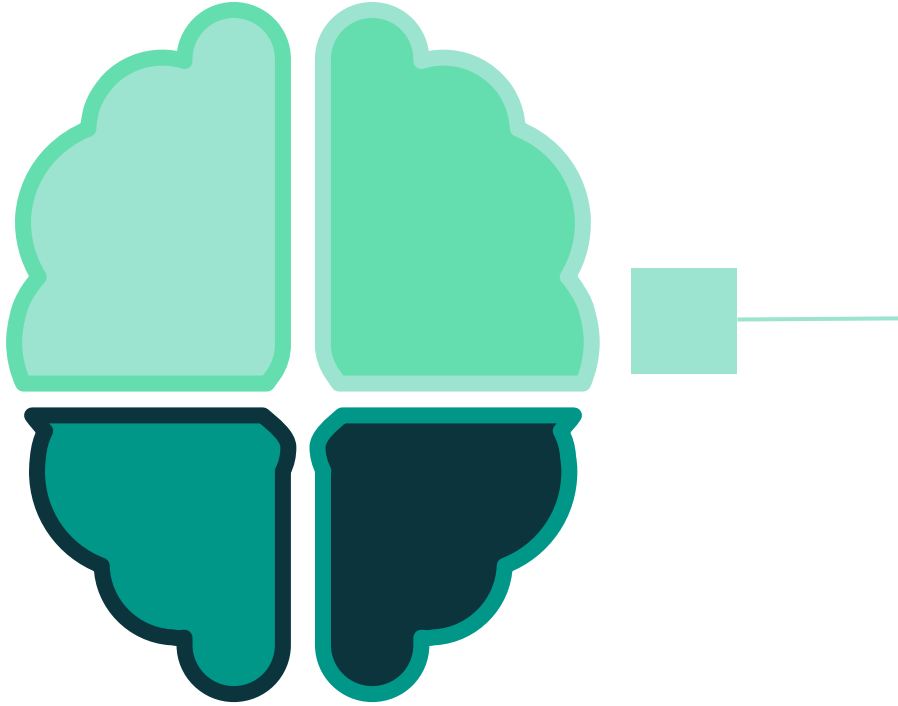

Choose EEG techniques despite the existence of better devices than other techniques.

# The Brain and Biological Neural Network

01


The billions of neurons in the human brain have highly complex firing patterns

02

Every interaction between these active neurons creates a minimal electrical discharge, which creates different amplitude and frequencies

03


Action potential

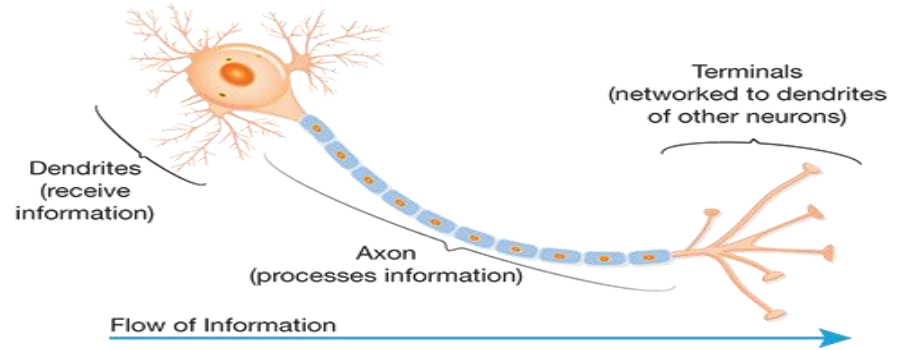

# The Ten-Twenty System

The international ten-twenty System of Electrode Placement uses on the Scalp to take signal.

---

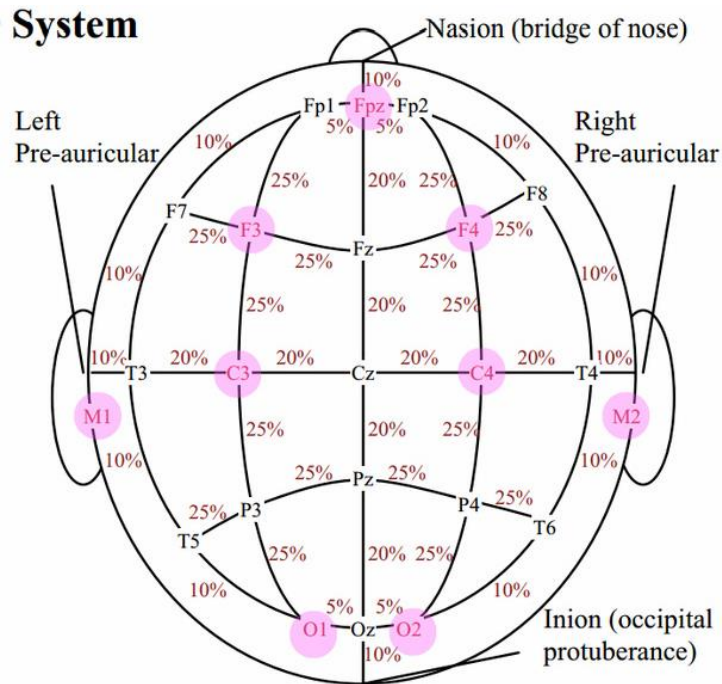

Each Channel name begin

It begin with one or two letters indicating to the general brain region

Each Channel name end

It is ended by the numbers that indicating the distance between channel and middle of the brain

# Muse & S-EEG Sensor

01


Muse



S-EEG Sensor

02

# Muse Headset

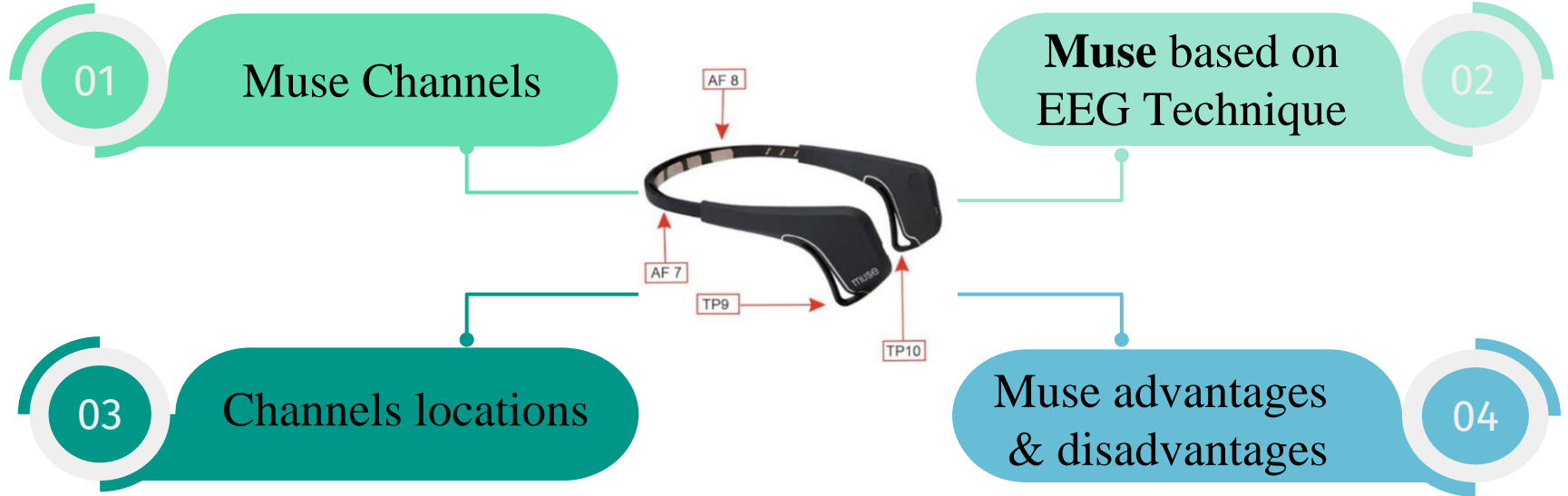



# S-EEG Sensor

S-EEG Sensor channel TP10, FPZ

S-EEG Sensor Advantages

S-EEG Sensor output



# Sensor Components

01

## amplifier

Because the signal is very small in mv

02

## Filters

Because the signals is very noisy.

03

## Notch Filter


To block 50 Hz

04

## ADC


To deal with the signal

## Input & output of each step

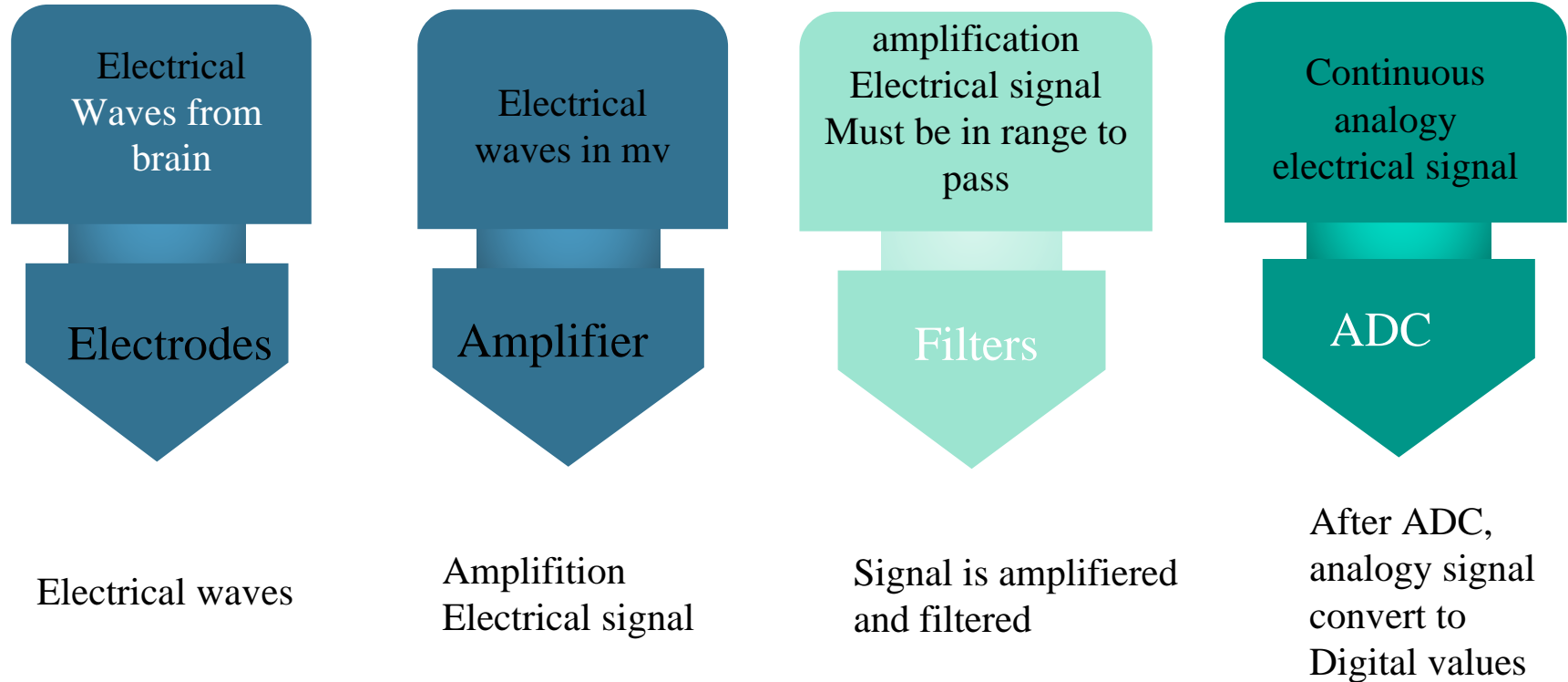

# Electrodes




01

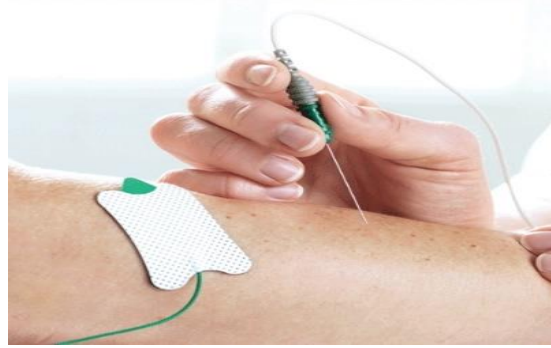

02

# Amplifier
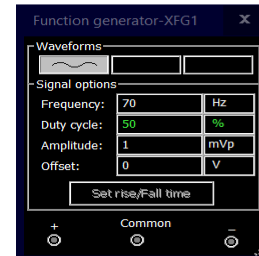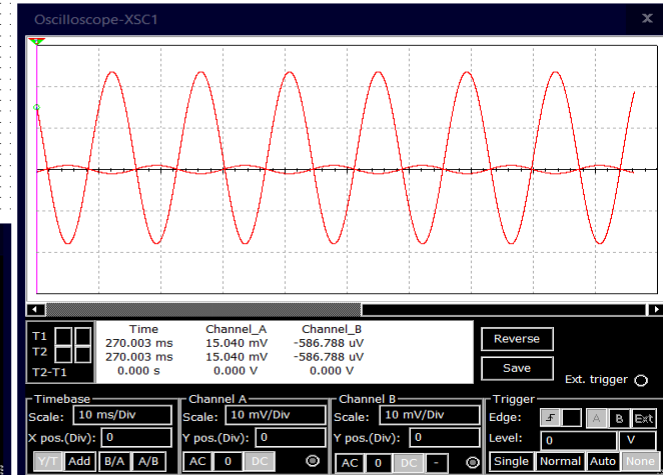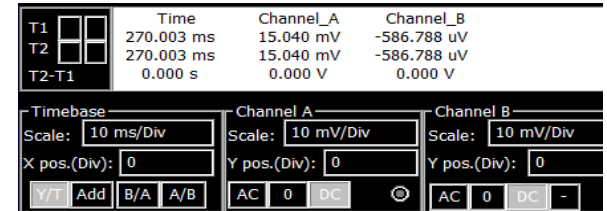
## The Final Output of instrumentation Amplifier




The instrumentation Amplifier that is extension of the difference amplifier in that it amplifies the difference between its input signal


# Filters

Band Pass Filter:  
To control in range  
that we need


From 1.5 hz to 318 hz

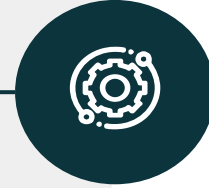

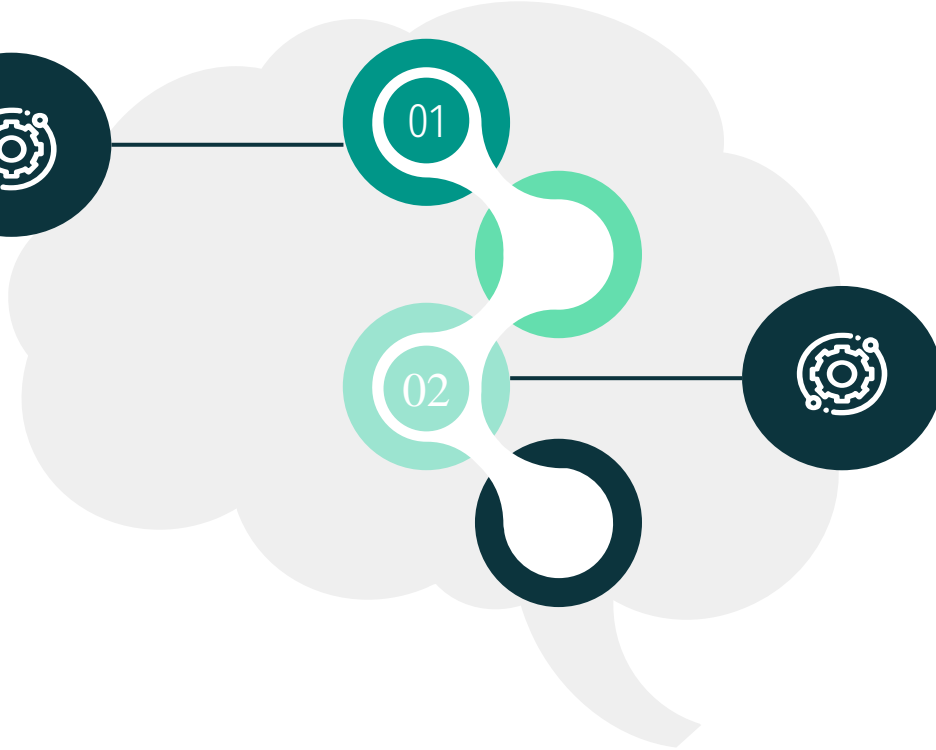Notch Filter:  
To block 50 Hz from  
our frequencies  
band






# Filter(Band Pass Filter)

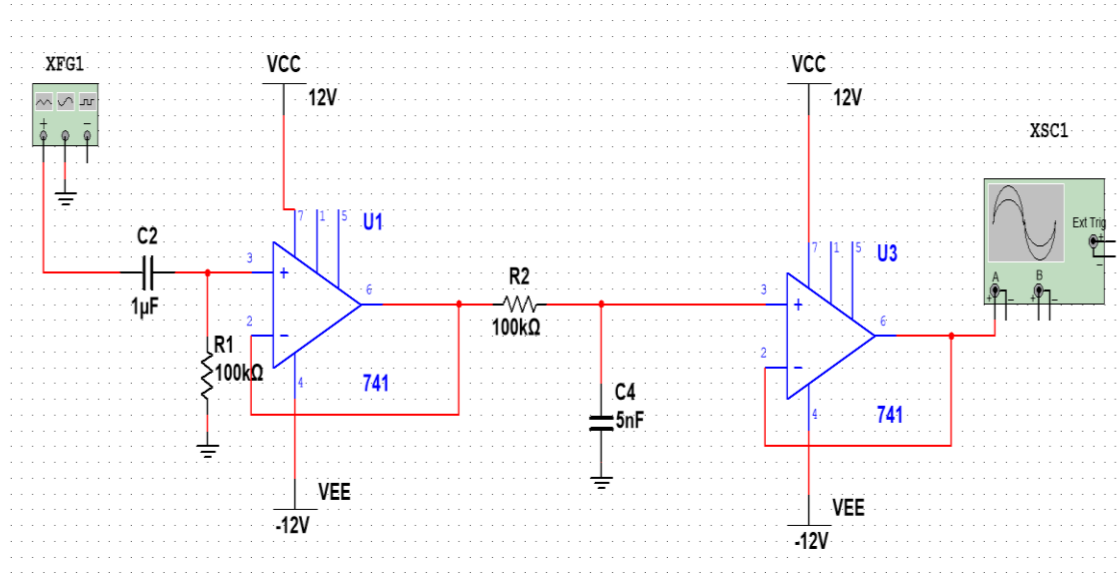


Band Pass Filter is used to detect range that we need From 1.5 HZ to 318 HZ

## The Final Output of Band pass Filter

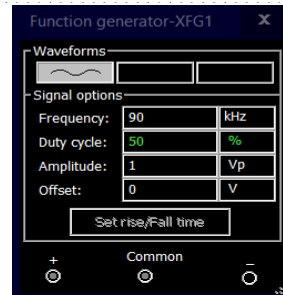
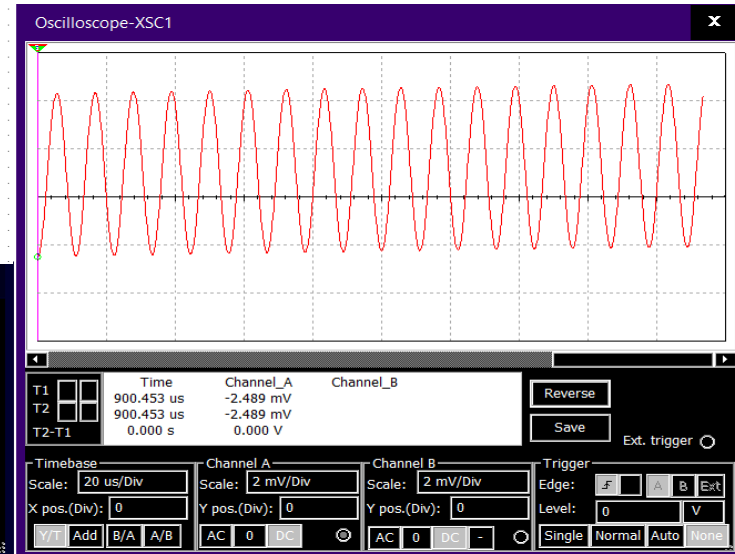
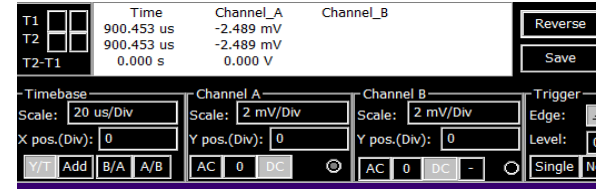


# Notch Filter

Notch Filter used to block 50 HZ

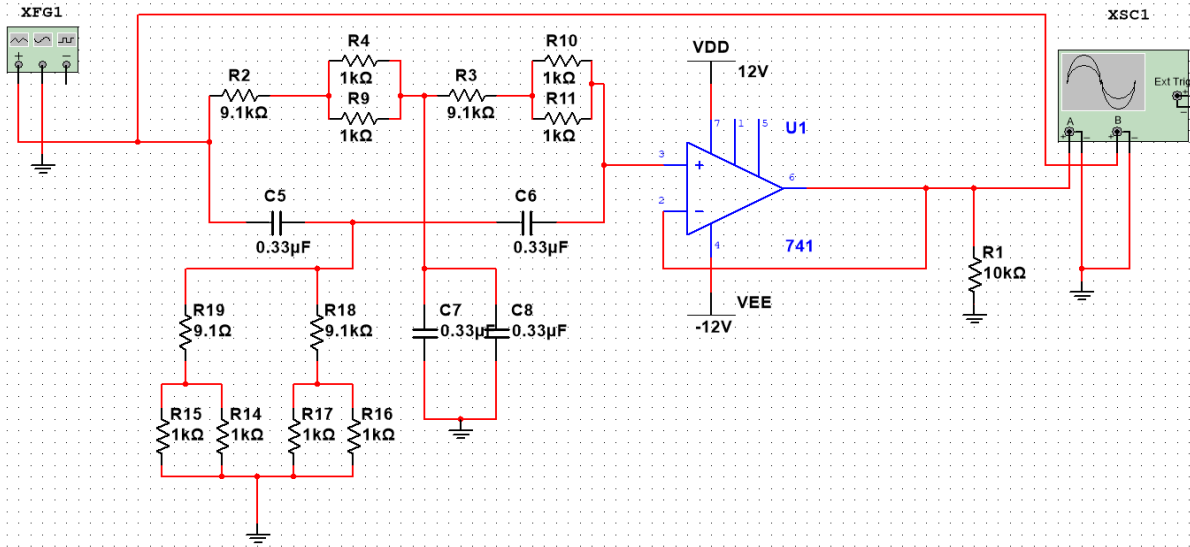


## The Final Output of Notch Filter

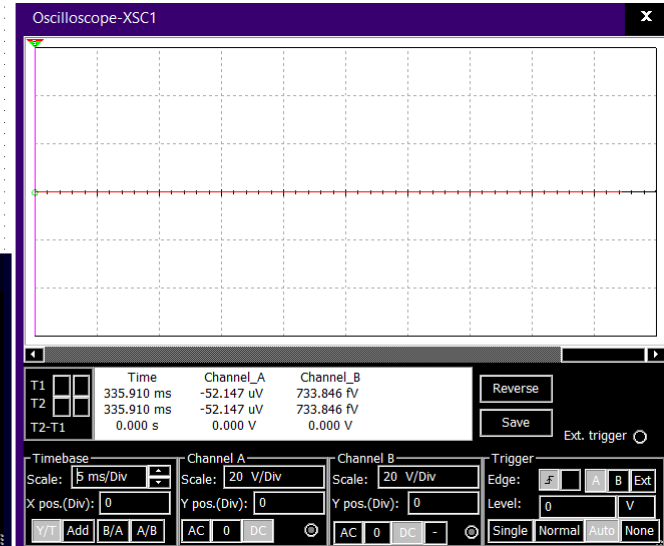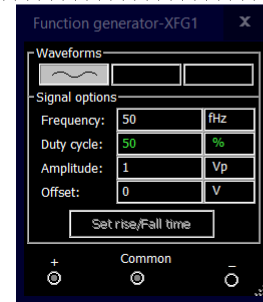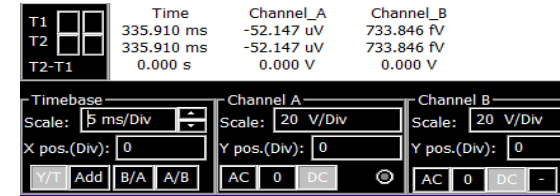



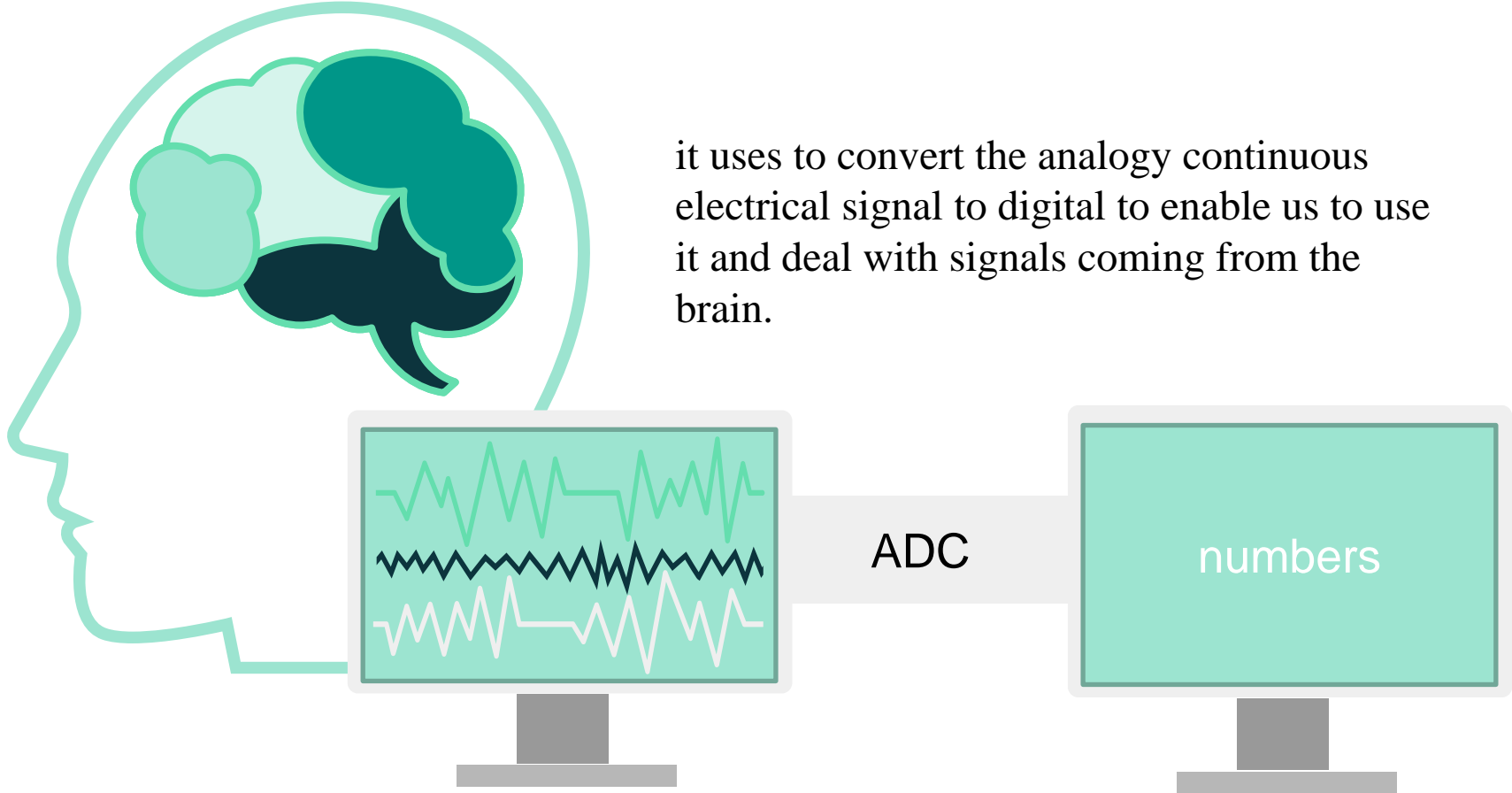
# ADC

it uses to convert the analogy continuous electrical signal to digital to enable us to use it and deal with signals coming from the brain.



# Brain Infographics


BreadBroad

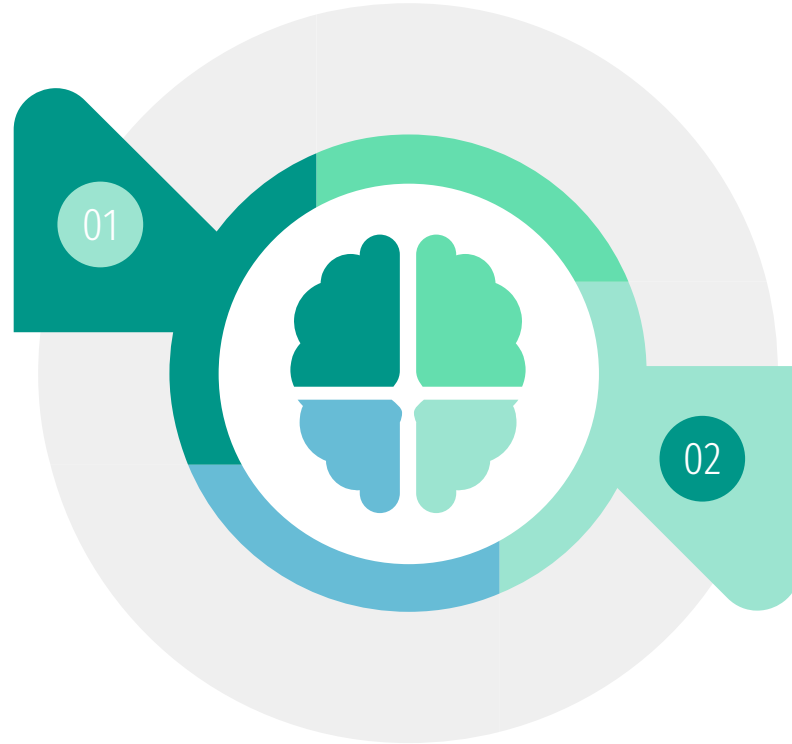


PCB

# BreadBroad:

01

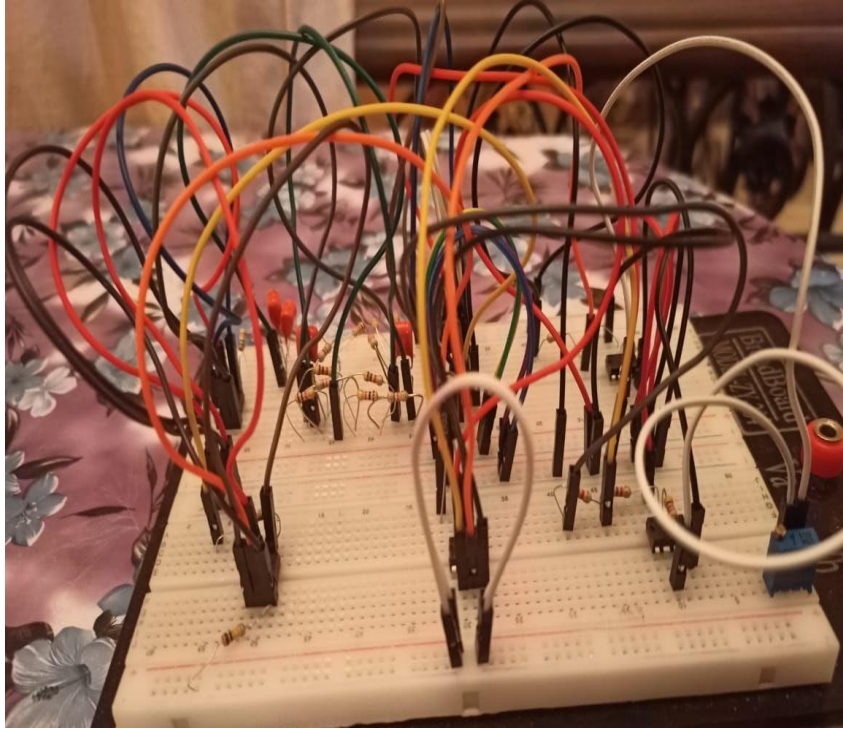


02

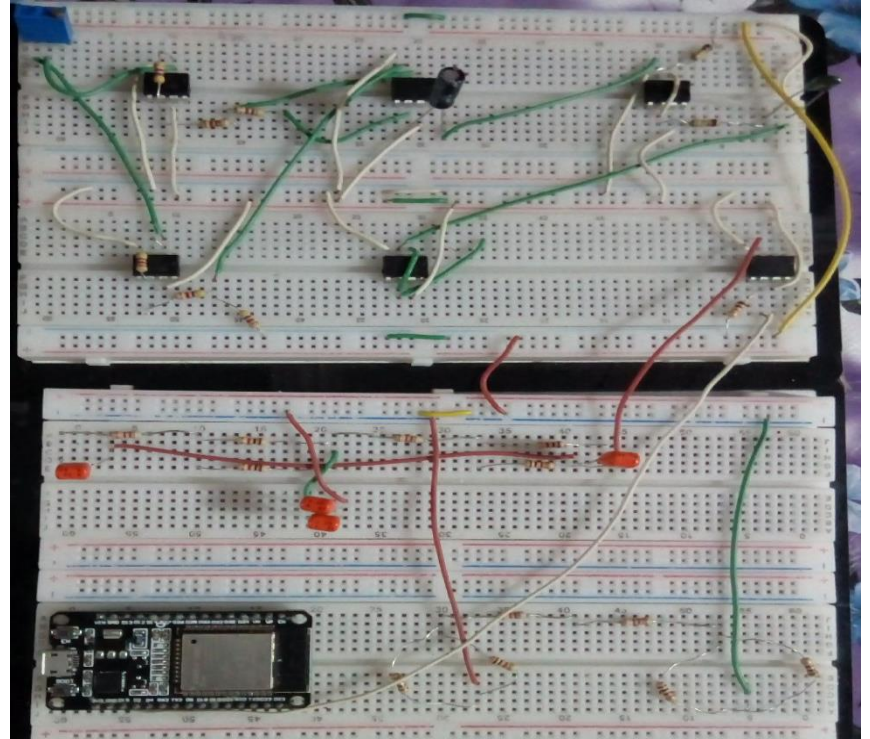

# The output of S-EEG Sensor




The output of eyes blink

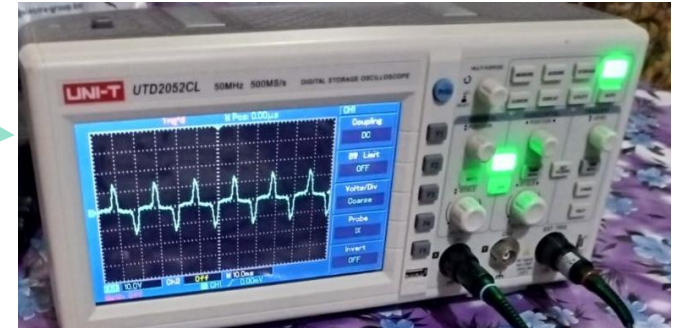



# 01 Proteus design

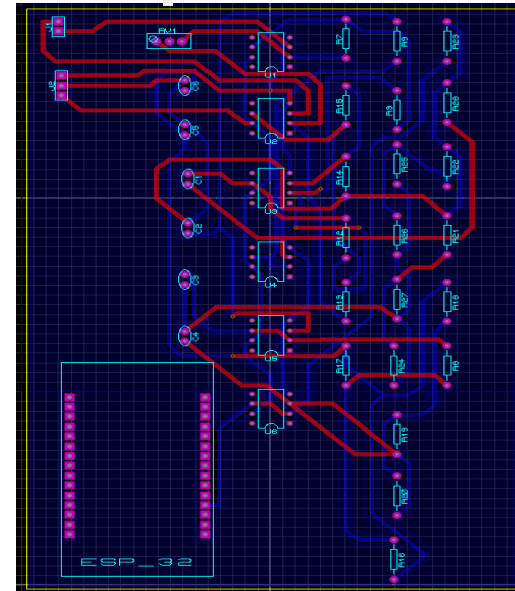

03

PCB

